

# Project report intergrated circuits

Sara Roberg Ghabeli, Sigurd Hagen Tullander

Fall 2020

# 1 Introduction

“Hello Dirty talk”

## 2 Theory

### 2.1 Analog circuit

The analog circuit has input signals delivered by the digital circuitry, and delivers its output to two ADCs. The analog circuit diagram is given in figure 1, where each of the four pixel block has the circuit given in figure 2.

 


Figure 1: Analog circuit schematic.

 


Figure 2: Pixel circuit schematic.

In detail, the analog circuit consists of 4 pixels in a 2x2 array. Each pixel in the same row shares the same NRE (Not-REad) input which means they are sending data to the ADC at the same time. Each pixel in the same column share the same active load and readout wire, which means they need to send data to the ADC at different times.

### 2.1.1 Conceptual operation of pixel circuit

Schematics for the pixel circuit is given in figure 2. It consists of a photo diode PD1, three switch transistors M1, M2 and M4, one buffer transistor M3 and a charge storage capacitor  $C_S$ . The photo diode is modeled by a diode and an ideal current source in parallel. The current source outputs a current  $I_D$  that is proportional to the illumination intensity on that particular pixel. This current is used to charge the transistor  $C_S$ . Ideally, we want that all of  $I_D$  flows through M1 and into  $C_S$  when EXPOSE is high and all of  $I_D$  flows back through the diode in the photo diode model when EXPOSE is low. In that way the voltage on node N2 when EXPOSE has been high for a time  $t$  is given by

$$V_{CS}(t) = \frac{1}{C_S} \int_0^t I_D(t) dt. \quad (1)$$

This means the voltage  $V_{CS}$  is proportional to the total illumination on the pixel throughout the exposure time, which is exactly what we want.

But since the camera is supposed to be reusable, we need a way to erase that charge before taking a new picture. That is what M2 is for. Ideally we want M2 to be a perfect switch, so that when ERASE is high,  $C_S$  is instantly uncharged through M2 and when ERASE is low, M2 does not conduct any current at all.

For the readout we do not want to connect N2 directly to OUT, since the output wire might

be very long and have a big capacitance. Instead, the voltage  $V_{CS}$  controls the conductance through a transistor M3. The higher  $V_{CS}$ , the lower conductance through M3 and higher voltage on OUT. In that way, the current required to control the voltage on the output wire is supplied through the active load in the top of each output wire, outside the pixel circuit.

But since all pixels in the same column share the same output wire we need a way to unconnect N3 from OUT, and that is what M4 is for. M4 is supposed to be an ideal switch so that the pixel is driving OUT only when NRE is low.

### 2.1.2 Dimensions for switch transistors

The transistors M1, M2 and M4 all function as switches, where a digital gate input decides whether the transistor should act as a short-circuit between drain and source, or as an open circuit. Since these transistors simply should have two possible states, it is key that the leakage current is minimized. This is particularly important for M1 and M2 to ensure that the voltage over  $C_s$  is as constant as possible during readout. In *Analog Circuit Design* by Tony Chan Carusone, one can read in section 1.4.1 that the subthreshold leakage current is given by

$$I_{off} = (n - 1)\mu_n C_{ox} \left(\frac{W}{L}\right) \left(\frac{kT}{q}\right)^2 \exp(-qV_t/nkT). \quad (2)$$

In order to minimize this leakage current,  $\frac{W}{L}$  need to be as small as possible, meaning the smallest possible width  $W$  and the largest possible length  $L$  is desired. The technology used will limit the possible width and length of the transistor, thus  $W$  and  $L$  can be chosen accordingly.

### 2.1.3 Value for $C_s$

To choose a suitable value for  $C_s$  spice simulations can be used. To know what values are the best we will look at the four corner cases for exposure time and light conditions. The corner cases will be denoted exposure-light, so for example max-min is maximum exposure time and minimum light. For each corner we will do a transient simulation. That means we will look at a graph that shows the voltage over  $C_s$  as a function of time. In each light-exposure corner, the resulting voltage value that we are interested in is the voltage over  $C_s$  at the end of the exposure. There are many possible approaches to how these corners should be tuned, and the one that we will apply is the following:

- Max-max corner should make  $C_s$  fully charged.
- Min-min corner should leave  $C_s$  uncharged.
- Min-max and max-min corners should make  $C_s$  half full charged.

The reason for why we want the corners to be like that is beyond the scope of this report.

### 2.1.4 Values for M3 and active load

Values for M3 and active load should be tuned using SPICE simulations for maximum dynamic range, but exact tuning will not affect very much since it is a very robust and self-regulating system.

## 2.2 Digital camera controller

The digital input signals in the analog circuit need to be controlled by a digital circuit - the digital camera controller.

### 2.2.1 Finite state machine

The wanted behaviour of the digital camera controller is described in the finite state machine (FSM) in figure 3.

 


Figure 3: The finite state machine for the digital camera controller.

In the FSM, there are three states. The camera starts in the *idle* state. In this state, the camera isn't in the process of taking any picture, so output signals *expose* and *ADC* should be LOW, and *NRE.1* and *NRE.2* should be HIGH. The camera should also prepare itself for a new picture in this state, so *erase* should be HIGH to erase any voltage from the potential previous exposure. The user should be able to adjust the exposure time with the signals *exp\_increase* and *exp\_decrease* in the *idle* state. These signals will respectively increase or decrease the exposure time with 1ms for each clock cycle they're HIGH to a minimum of 2ms and a maximum of 30ms. When the signal *init* is HIGH, which happens when the user presses the shutter button on the camera, the camera will enter the *exposure* state. The

exception is if the *rst* input signal is **HIGH**. In any state, *rst* being **HIGH** should override any process and take the camera back to *idle*.

When the camera is entering the *exposure* state, *erase* should be set **LOW** and *expose* should be set **HIGH** to begin the exposure. An internal register *cnt* should hold the exposure time as a number of clock cycles, and decrement for each clock cycle. If *rst* is **HIGH** at any time during *exposure*, the camera should return to the *idle* state. When the *cnt* register has reached 0, the camera should enter the *readout* state if *rst* is **LOW**.

The *readout* state is the final state, in which the data from the individual pixels are read and inputted in the ADC. First, *expose* should be set **LOW** since the exposure is done. Then, *NRE\_1* should be **LOW** first at the same time as *ADC* is **HIGH**, to read from the top two pixels and input it to the ADC. Lastly, *NRE\_2* should be **LOW** at the same time as *ADC* is **HIGH** to do the same for the bottom two pixels. Exactly how the output signals should be will be properly explored in the next section. As with the *exposure* state, *rst* being **HIGH** at any time should return the camera to *idle*.

### 2.2.2 Output timing

### 2.2.3 Module interface

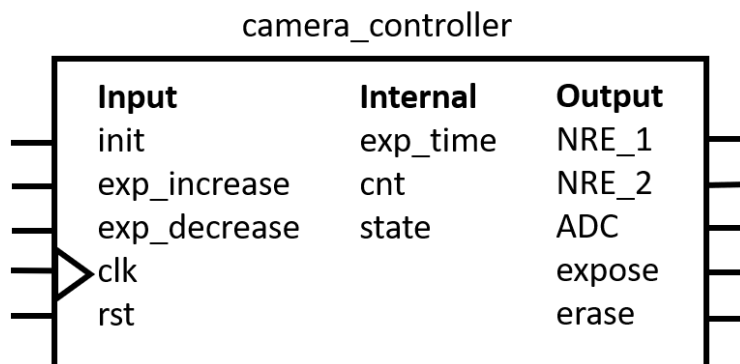


Figure 4: Overview of input and output pins as well as internal registers for the camera controller module.

## 3 Results

### 3.1 Analog pixel circuit

#### 3.1.1 Values and dimensions

The transistor technology used limits the width to

 


Figure 5: Minimum exposure time - minimum light

 


Figure 6: Minimum exposure time - maximum light

$$1.08\mu\text{m} \leq W \leq 5.04\mu\text{m} \quad (3)$$

and limits the length to

$$0.36\mu\text{m} \leq L \leq 1.08\mu\text{m}. \quad (4)$$

As explained in section 2.1.2, the length and width of the switch transistors will be  $1.08\mu\text{m}$ .

CS was tuned to 2pF. The output from simulations with this value for the exposure-light corners min-min, min-max, max-min and max-max are shown respectively in figures 5, 6, 7 and 8.



 


Figure 7: Maximum exposure time - minimum light


 


Figure 8: Maximum exposure time - maximum light

 

### 3.1.2 Analog circuit simulation

### 3.2 Digital circuit

### 3.2.1 Digital circuit simulation

Explaining the big waveform.

## 4 Discussion